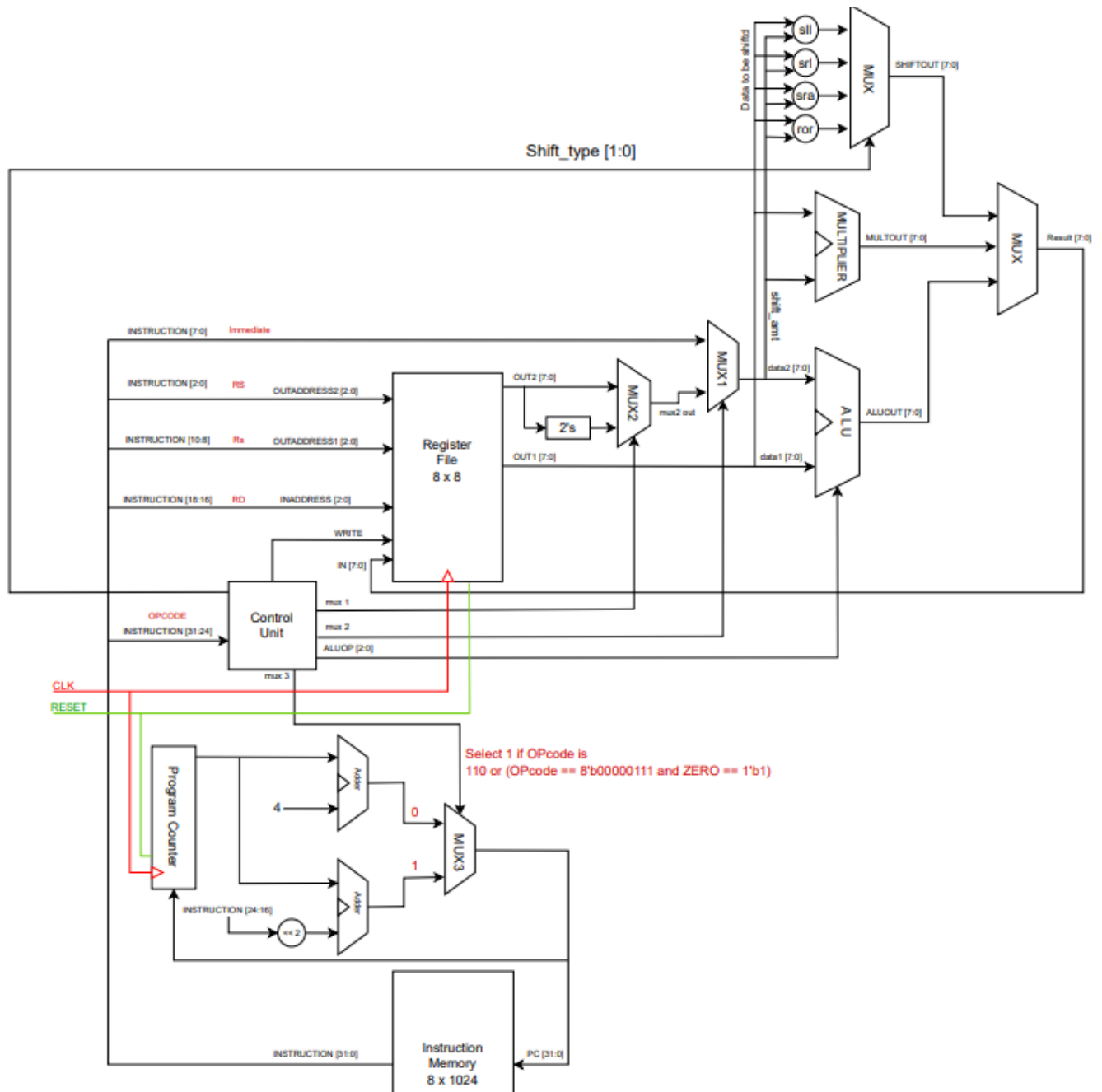



The Big Picture of the Simple 8-Bit Computer

Here is the complete block diagram of a simple 8-bit computer which performs the **add**, **sub**, **and**, **or**, **beq**, **j**, **mult**, **sll**, **srl**, **sra**, **ror**, **bne** instructions. So this can be used to perform different algorithms to find factorial of a number, n^{th} fibonacci number, et cetra. So lets dive into the implementation of mult, sll, srl, sra, ror, bne instructions...



Implementation of **mult, ssl, srl, sra, ror, bne** instructions...

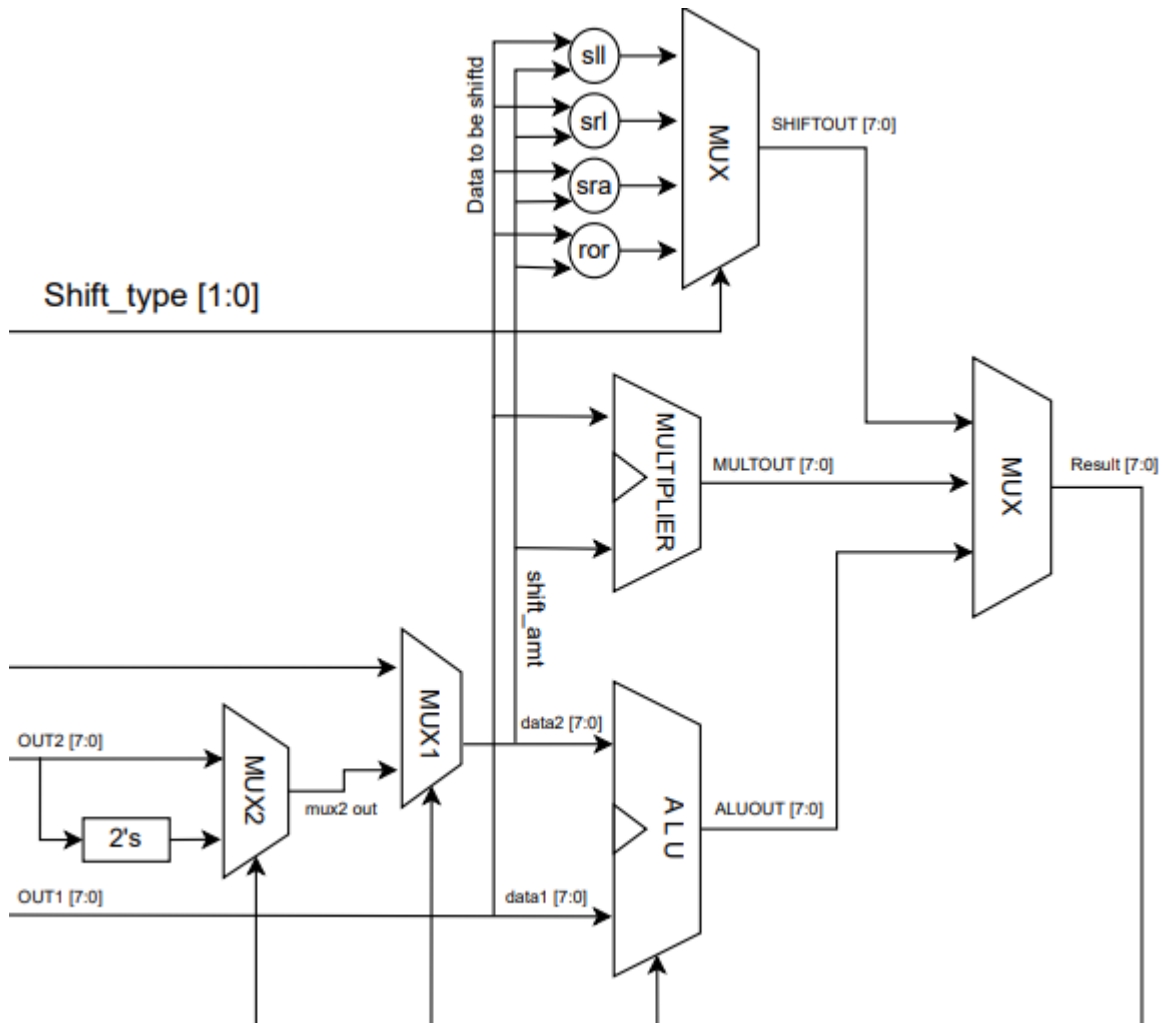
Additional two units have been introduced to perform shift and multiplication operations. Shift module has 4 sub units and a multiplexer to select shift_type. And there is another multiplexer to select the result from shift, ALU or Multiplier based on the instruction. Selection signals come from the control unit.



Multiplier

A delay of #2 is added for the multiply operation.

Circuit Diagram

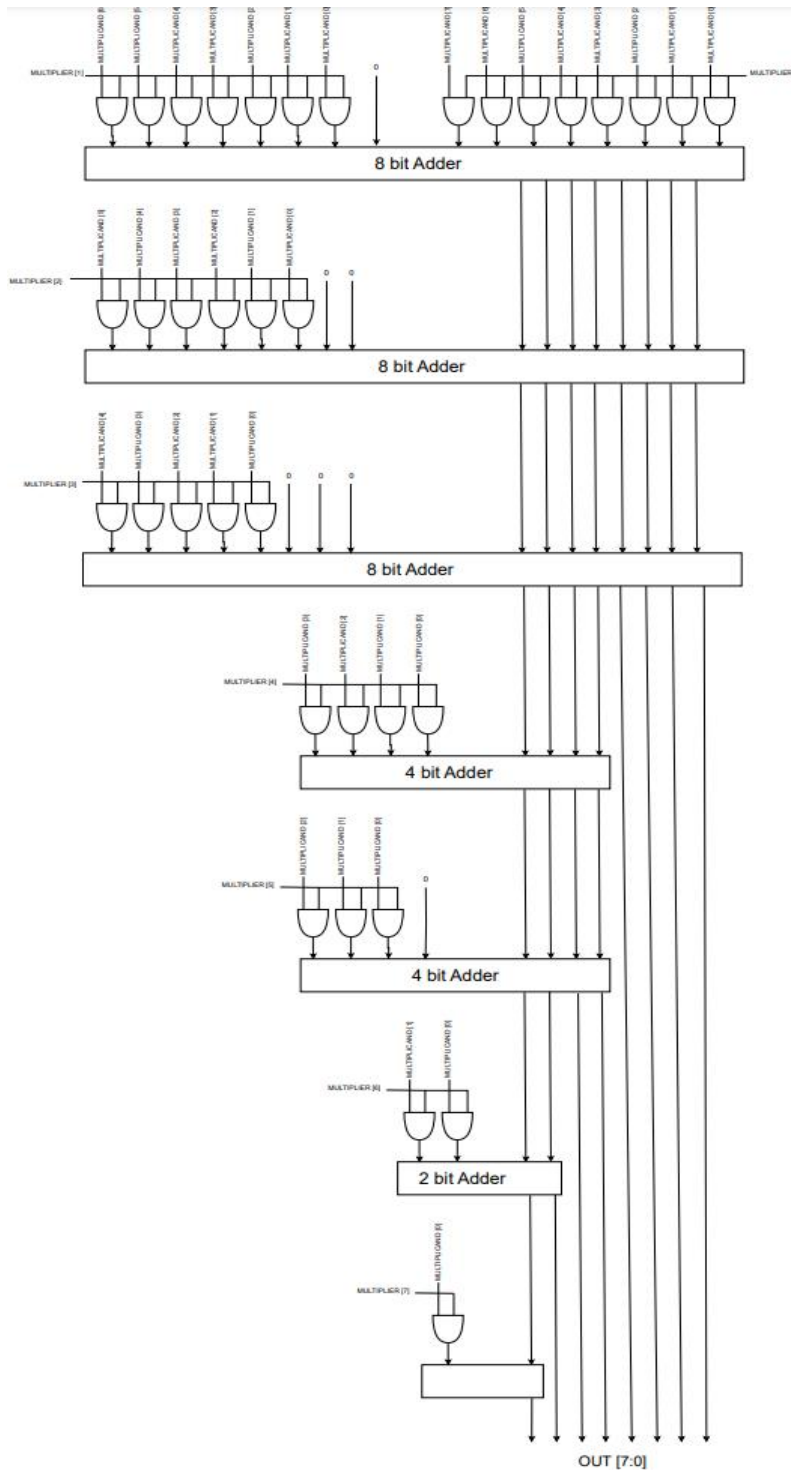

Verilog Code


```

module multiplier #(
    parameter W = 8
) (
    input  [W-1:0] MULTIPLICAND,
    input  [W-1:0] MULTIPLIER,
    output [W-1:0] OUT
);
    // normal multiplication as we do on decimal numbers
    assign #2 OUT = {MULTIPLICAND*MULTIPLIER[0]    } +
        {MULTIPLICAND*MULTIPLIER[1],1'b0} +
        {MULTIPLICAND*MULTIPLIER[2],2'b00} +
        {MULTIPLICAND*MULTIPLIER[3],3'b000} +
        {MULTIPLICAND*MULTIPLIER[4],4'b0000} +
        {MULTIPLICAND*MULTIPLIER[5],5'b00000} +
        {MULTIPLICAND*MULTIPLIER[6],6'b000000} +
        {MULTIPLICAND*MULTIPLIER[7],7'b0000000};

Endmodule

```


Waveforms

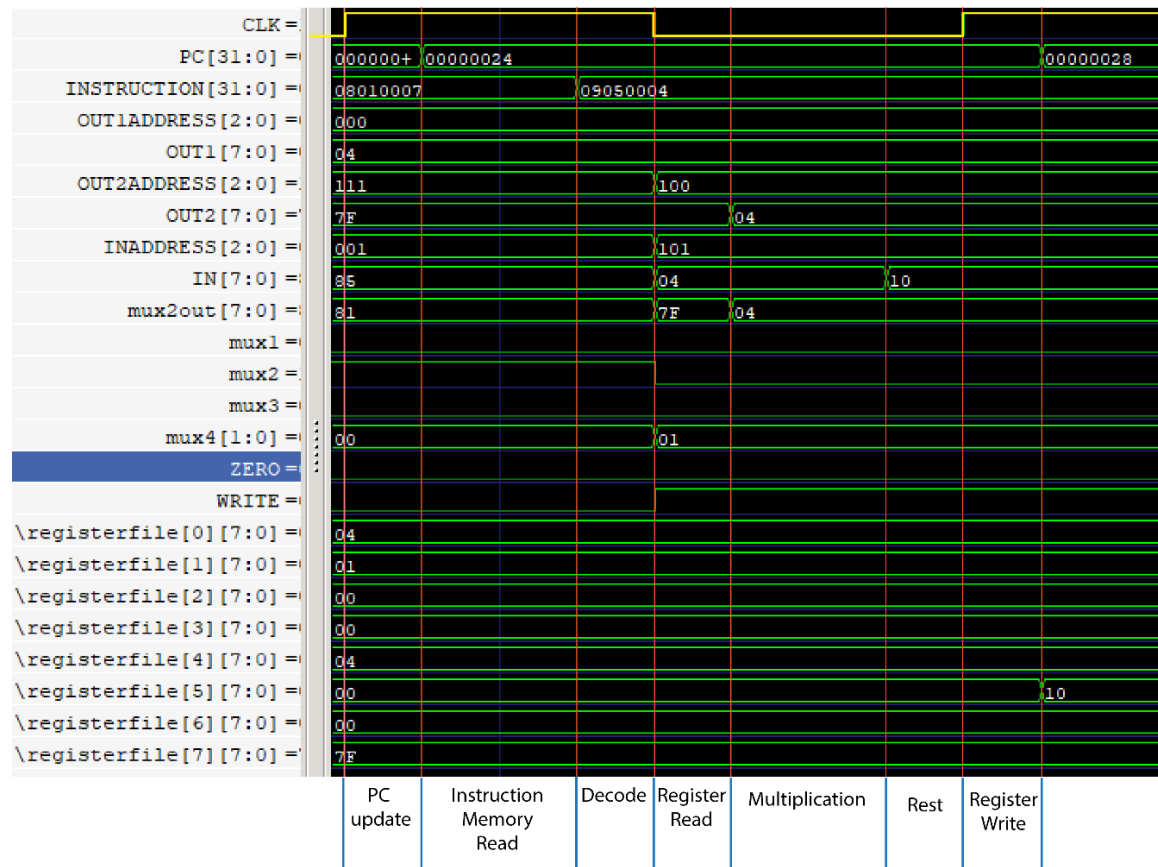

Shift

As shown below I have added new functional units for shifting and to select what type of shift is needed to perform based on the instruction. **Shift_type [1:0]** signal comes from the control unit.

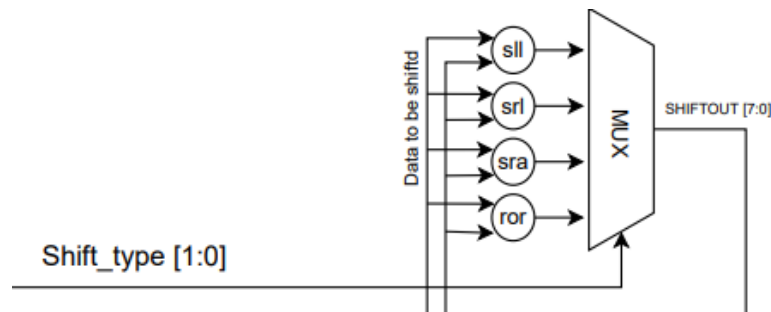
A delay of **#3** is added for the shift operation.




Verilog Code

```
module shift #(
    parameter W = 8
) (
    input      [W-1:0] data,
    input      [W-1:0] shift_amt,
    input      [1:0] shift_type,
    output reg  [W-1:0] result
);
    integer i;
    always @(*) begin
        #3
        result = data;
        case(shift_type)
            2'b00: begin // LSL
                    for (i=0;i<shift_amt;i = i+1) result = {result[W-2:0], 1'b0};
                    end
            2'b01: begin // LSR
                    for (i=0;i<shift_amt;i = i+1) result = {1'b0, result[W-1:1]};
                    end
            2'b10: begin // SRA
                    for (i=0;i<shift_amt;i=i+1) result = {data[W-1], result[W-
1:1]};
                    end
            2'b11: begin // ROR
                    for (i=0;i<shift_amt;i=i+1) result = {data[0], result[W-
1:1]};
                    end
        endcase
    end
endmodule
```


Waveform for logical shift left (sll)

 


Waveform for logical shift right (srl)

 

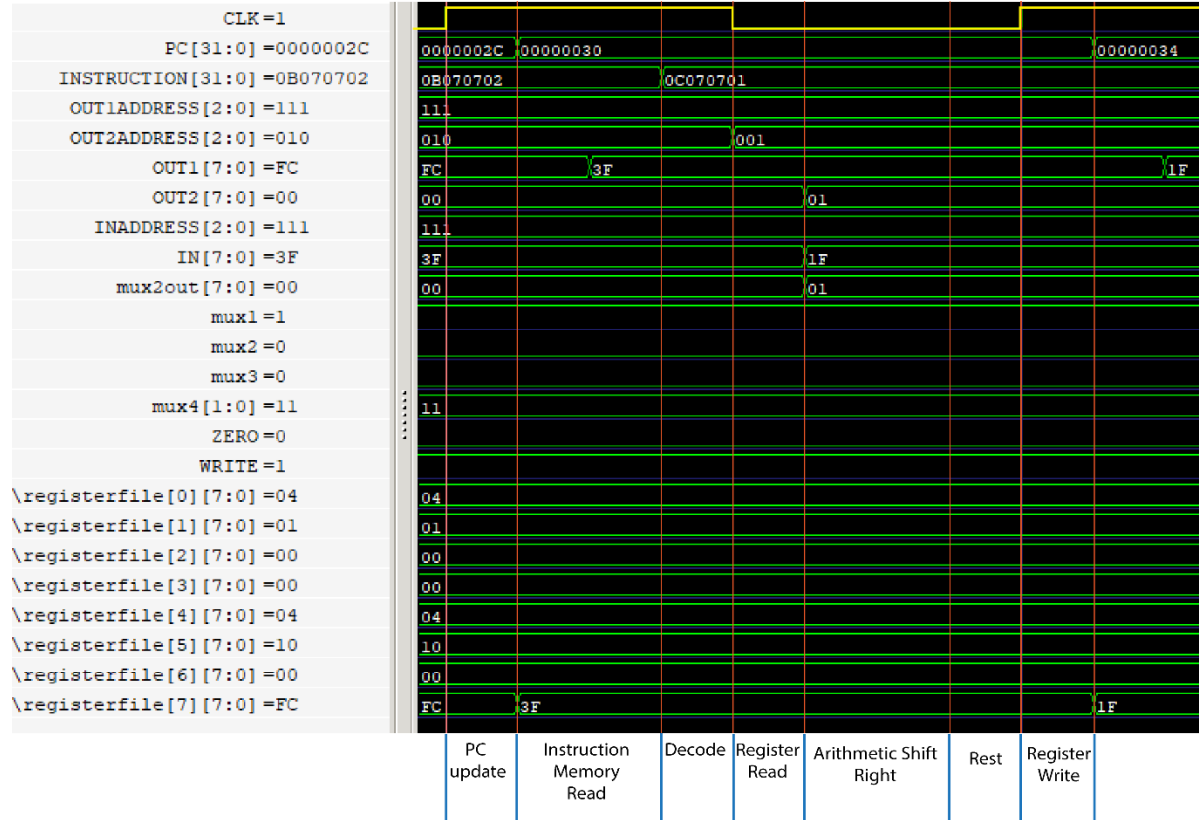Waveform for arithmetic shift right (sra)




Waveform for rotate right (ror)

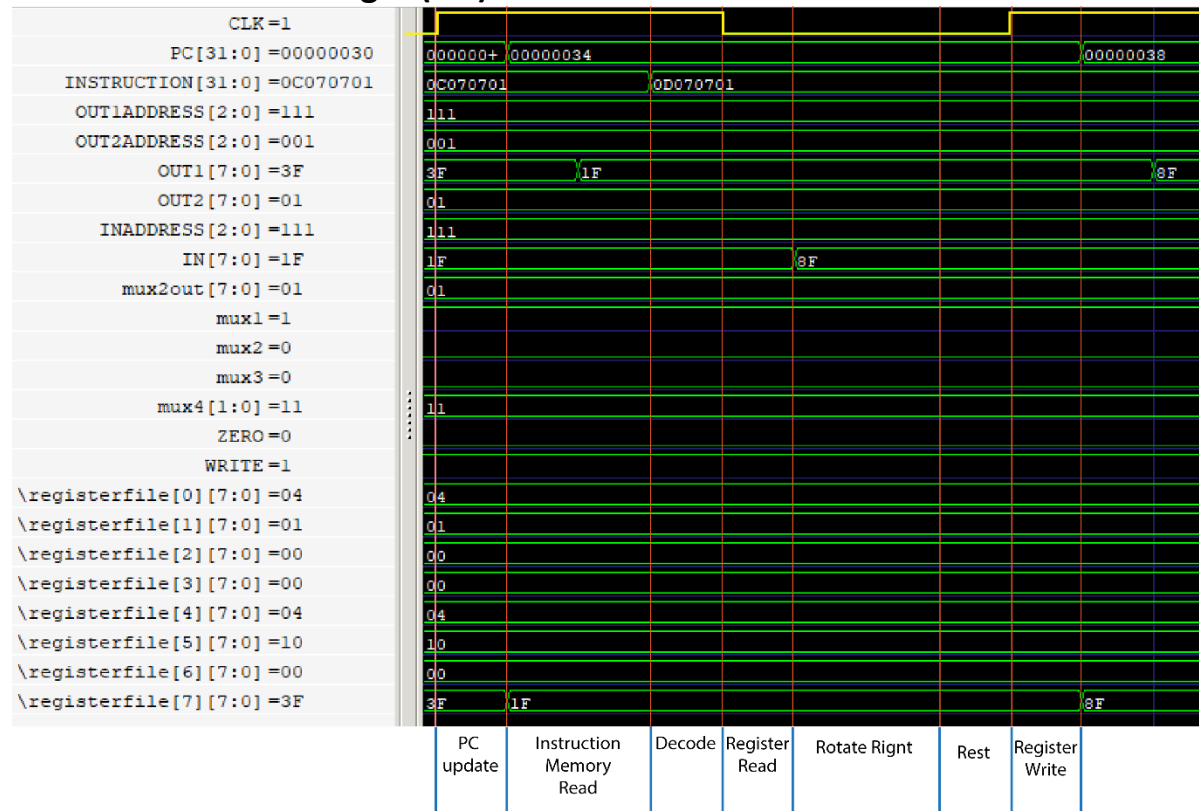

Bne instruction

For **bne** instruction we did a small modification for **beq** instruction. When we call **beq** control unit checks whether the given two registers equal or not and it indicates by a signal called **ZERO**. If **ZERO** = 1, given two registers are equal otherwise not equal. So if **ZERO** = 0 and instruction = 8'b00001000 then **bne** should execute.


Waveform for branch not equal (bne)

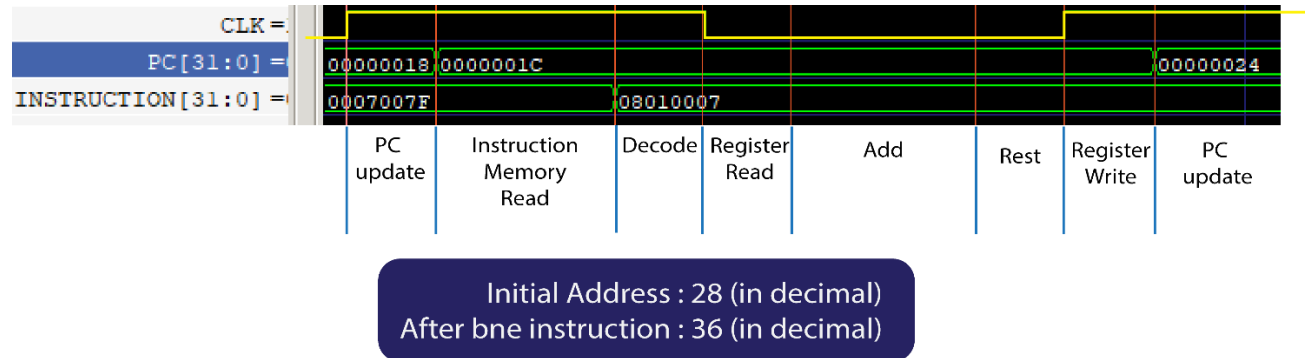

Here is the sample assembly code that we used for testing purpose,

| // Assembly program | // binary instructions |
|---------------------|-------------------------------------|
| loadi 0 0x00 | 00000000 00000000 00000000 00000000 |
| loadi 1 0x01 | 00000001 00000000 00000001 00000000 |
| loadi 4 0x04 | 00000100 00000000 00000100 00000000 |
| beq 0x2 0 4 | 00000100 00000000 00000010 00000111 |
| add 0 0 1 | 00000001 00000000 00000000 00000001 |
| j 0xFD | 00000000 00000000 11111101 00000110 |
| loadi 7 0xFF | 01111111 00000000 00000111 00000000 |
| bne 0x01 0 7 | 00000111 00000000 00000001 00001000 |
| loadi 6 0xFF | 11111111 00000000 00000110 00000000 |
| mult 5 0 4 | 00000100 00000000 00000101 00001001 |
| sll 7 7 0x02 | 00000010 00000111 00000111 00001010 |
| srl 7 7 0x02 | 00000010 00000111 00000111 00001011 |
| sra 7 7 0x01 | 00000001 00000111 00000111 00001100 |
| ror 7 7 0x01 | 00000001 00000111 00000111 00001101 |

 Variation of Register Values for the above program,



Instruction Formats

| | | | |
|------------------|-----------------|----------------|---------------|
| add (bits 31-24) | Rd (bits 23-16) | Rt (bits 15-8) | Rs (bits 7-0) |
| OPCODE:0000_0000 | | | |

| | | | |
|------------------|-----------------|----------------|---------------|
| add (bits 31-24) | Rd (bits 23-16) | Rt (bits 15-8) | Rs (bits 7-0) |
| OPCODE:0000_0001 | | | |

| | | | |
|------------------|-----------------|----------------|---------------|
| sub (bits 31-24) | Rd (bits 23-16) | Rt (bits 15-8) | Rs (bits 7-0) |
| OPCODE:0000_0100 | | | |

| | | | |
|------------------|-----------------|----------------|---------------|
| and (bits 31-24) | Rd (bits 23-16) | Rt (bits 15-8) | Rs (bits 7-0) |
| OPCODE:0000_0010 | | | |

| | | | |
|------------------|-----------------|----------------|---------------|
| orr (bits 31-24) | Rd (bits 23-16) | Rt (bits 15-8) | Rs (bits 7-0) |
| OPCODE:0000_0011 | | | |

| | | | |
|------------------|----------------------|----------------|---------------|
| beq (bits 31-24) | Addr>>2 (bits 23-16) | R1 (bits 15-8) | R2 (bits 7-0) |
| OPCODE:0000_0111 | | | |

| | | | |
|------------------|----------------------|---------------|--------------|
| j (bits 31-24) | Addr>>2 (bits 23-16) | - (bits 15-8) | - (bits 7-0) |
| OPCODE:0000_0110 | | | |

| | | | |
|-------------------|-----------------|----------------|---------------|
| mult (bits 31-24) | Rd (bits 23-16) | Rt (bits 15-8) | Rs (bits 7-0) |
| OPCODE:0000_1001 | | | |

| | | | |
|------------------|-----------------|----------------|----------------------|
| sll (bits 31-24) | R1 (bits 23-16) | R2 (bits 15-8) | Shift_amt (bits 7-0) |
| OPCODE:0000_1010 | | | |

| | | | |
|------------------|-----------------|----------------|----------------------|
| srl (bits 31-24) | R1 (bits 23-16) | R2 (bits 15-8) | Shift_amt (bits 7-0) |
| OPCODE:0000_1011 | | | |

| | | | |
|------------------|-----------------|----------------|----------------------|
| sra (bits 31-24) | R1 (bits 23-16) | R2 (bits 15-8) | Shift_amt (bits 7-0) |
|------------------|-----------------|----------------|----------------------|

OPCODE:0000_1100

| | | | |
|------------------|-----------------|----------------|----------------------|
| ror (bits 31-24) | R1 (bits 23-16) | R2 (bits 15-8) | Shift_amt (bits 7-0) |
|------------------|-----------------|----------------|----------------------|

OPCODE:0000_1101

| | | | |
|------------------|----------------------|----------------|---------------|
| bne (bits 31-24) | Addr>>2 (bits 23-16) | R1 (bits 15-8) | R2 (bits 7-0) |
|------------------|----------------------|----------------|---------------|

OPCODE:0000_1000*********END OF THE DOCUMENT**